

Mark schemes

1.


(a)

Inputs			Output
C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

All Q states correct for 1 mark

1

(b)

 

Correct orientation for resistor & switch ✓

Correct tap-off point for X ✓

2

(c)

$$Q = \overline{(C \cdot A) + (C \cdot B)}$$

Two correct brackets ✓

+ with full bar ✓

Allow for 1 mark: $Q = \overline{C \cdot (A + B)}$

2

(d) The gate acts as an inverter ✓

Accept 'NOT' as the function

1

(e) Must be a reason and a consequence for the mark. ✓

eg Uses only one type of logic gate so need to hold less stock

OR

Uses only one chip rather than two so circuit board can be smaller / less power needed / cheaper

Do not allow: Less complex circuit

1

[7]

2.

- (a) +ve knee develops at 0.7 V and does not exceed 1.5 V at 30 mA ✓
 -ve knee develops at 5.1 V; 5 mA with near vertical drop. Does not exceed – 5.5 V at –30 mA ✓

2

- (b) Zener diode provides a reference voltage for non-inverting input ✓

Or

Zener diode provides a stabilised voltage for non-inverting input ✓

Accept combination of the two statements

1

- (c) $I = V/R = 3.9 \text{ V} / 100 \Omega = 39 \text{ mA}$

This is larger than the minimum current to make Zener diode work so the resistor value is fine. ✓

$$P = I^2 R = (39 \times 10^{-3})^2 \times 100 = 0.152 \text{ watts}$$

This is greater than the power rating for the resistor, so is not a suitable power rating for the resistor ✓

Ecf from value of I

2

- (d) The reference voltage at the non-inverting input is now smaller ✓

This will cause the output **W** to switch at a lower light intensity than before ✓

2

- (e) $Q = \overline{(X + Y)} \cdot W$ ✓

Accept transformations eg

$$Q = \overline{X} \cdot (\overline{Y + W})$$

$$Q = \overline{X} \cdot Y \cdot \overline{W}$$

1

- (f) MOSFET has large input impedance

OR

MOSFET causes no loading of the logic gate output. ✓

1

[9]

3. (a)


Number shown on die	Logic inputs			Logic outputs						
	C	B	A	L1	L2	L3	L4	L5	L6	L7
1	0	0	0	0	0	0	0	0	0	1
2	0	0	1	1	0	0	0	0	1	0
3	0	1	0	1	0	0	0	0	1	1
4	0	1	1	1	0	1	1	0	1	0
5	1	0	0	1	0	1	1	0	1	1
6	1	0	1	1	1	1	1	1	1	0
Reset 6 → 1										

One mark for each full pattern of L1 and L6:

2

(b) L7 = NOT A; Accept: $L7 = \bar{A}$

1

 


1 mark for reset condition from B and C

1 mark for use of a single 2-input AND gate

(accept correct implementation of the full reset code $\bar{A}.B.C$ for 1 mark)

2

(d)

 

1 mark - NOT gate from B:

1 mark - AND gate from \bar{B} and C:

1 mark - OR gate connecting the two conditions:

3

[8]

4.


(a) $PRF = 1 / (1.4 RC)$

$= 1 / (1.4 \times 5.1 \times 10^3 \times 10 \times 10^{-9})$

14 kHz ✓

1

 (b) Square wave with correct phase and amplitude ✓



1

(c) New resistor calculated and stated to be 1.7 kΩ ✓

New resistor placed in parallel with original resistor ✓

Ecf from part (a)

2

(d) $T = \frac{1}{f} = \frac{1}{5 \times 10^3} = 0.2 \text{ ms (200 } \mu\text{s)}$

$$t_C = 0.2 \times 10^{-3} \times \frac{3}{4} = 150 \mu\text{s}$$

$$t_D = 0.2 \times 10^{-3} \times \frac{1}{4} = 50 \mu\text{s}$$

$$R_2 = \frac{t_D}{0.7 \times C} = \frac{50 \times 10^{-6}}{0.7 \times 10 \times 10^{-9}} = 7.1 \text{ k}\Omega \text{ (Accept 7k}\Omega\text{)}$$

$$R_1 = \frac{t_C}{0.7 \times C} - R_2 = 14.3 \text{ k}\Omega \text{ (Accept 14k}\Omega\text{)}$$

1 mark for significant calculation

Eg showing $R_1 = 2R_2$

OR

Calculation for t_C or t_D

1 mark for values of R_1 and R_2

2

(e) Two properties per mark – (max mark 2)✓✓


- A square wave
- Amplitude of 0 V to 5 V
- Periodic time of 0.2 ms
- High for 0.15 ms – Low for 0.05 ms

2

[8]

5.


(a)

 

Flat line of Q₀ - 1 mark

Correct fall of Q₁ and rise of Q₂ - 1 mark

2

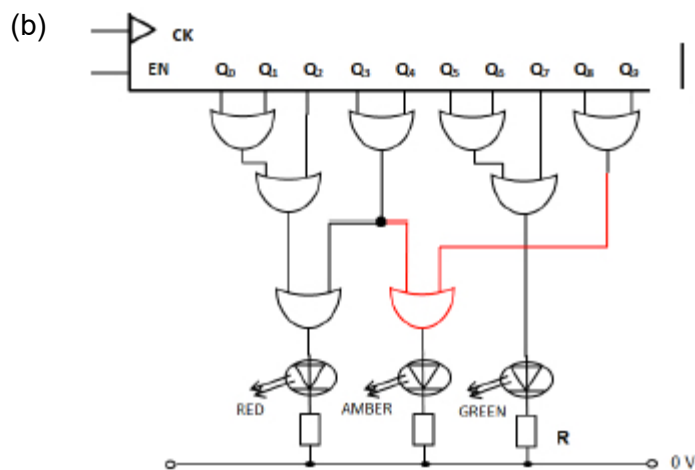

Logic OR gate correctly connected in position for 1 mark

1

(c) The ON time for the green LED is determined by:

the frequency of the clock ✓

the number of adjacent outputs that are OR'ed ✓

Accept reference to the period of the clock pulse.

2

(d) $R = V_R / I$; $R = (9 - 2.1) V \checkmark / 9 \text{ mA}$

$R = 6.9 V / 9 \text{ mA}$; $R = 767 \Omega \checkmark$

Minimum resistor value that can be used in order not to exceed 9 mA is 767 Ω .

The 720 Ω resistor range is (684 to 756) Ω and falls below this value so should not be used. ✓

OR

Calculation using 720 $\Omega \pm 5\%$ Resistor range = (684 to 756) $\Omega \checkmark$ leading to smallest current of 9.1 mA ✓

This current will exceed the permitted value of 9 mA. Don't use. ✓

1 One mark for voltage across the resistor

2 One mark for a suitable I-V-R calculation

3 One mark for conclusion with reason.

Use of error range to give max resistance must be seen in either 2 or 3 for that mark to be awarded.

3

[8]

6. (a) $Q = (\bar{A}.B) + (A.\bar{B})$ ✓✓ (allow written format)
 Do not allow $(A \oplus B)$

- Correct two terms ✓
- Correct operator for OR gate ✓

2

(b)

B	A	C	D	E	F	Q
0	0	1	1	0	0	0
0	1	0	1	0	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0

✓ ✓

Correct column C
Correct column E

2

(c) Any two criteria ✓✓

- Less complex circuit – easier to manufacture
- Only uses one type of chip – more economical to buy
- Uses fewer ICs so saves space
- Uses fewer ICs so saves on power consumption

Accept any other valid reason

2


(d) EOR ✓

Also allow EXOR, XOR

1

[7]

7. (a)

 

Correct logic gate to MR ✓
 Q₃ to logic gate input ✓
 Midpoint of switch chain to logic gate input ✓

OR

Accept 2 diodes in correct position ✓✓ Correct orientation ✓
 2 marks only for both resets in correct positions but no logic gate.
 1 mark only for any correct single reset circuit.

3

(b) $(A \cdot C) \checkmark + (B \cdot \bar{C}) \checkmark$

Second mark includes the (+)
 Also allow commutative equivalents such
 as $(B \cdot \bar{C}) + (A \cdot C)$

2

(c)

Decimal number	C	B	A	D	E	F	W
0	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
2	0	1	0	1	0	1	1
3	0	1	1	1	0	1	1
4	1	0	0	0	0	0	0
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1


1

(d) numbers 2, 4 and 6 ✓

accept even numbers

1

(e)

 

NOT A into the AND gate ✓

(B OR C) into the AND gate ✓

Only 1 mark if AND gate is incorrect

Do not accept use of NAND, NOR, EXOR / EXNOR gates to generate equivalent functions.

2

[9]

8.

- (a) Difference: BCD counter outputs binary codes. A Johnson decade counter outputs a single output sequentially ✓

Similarity: Both counters recycle at the 10th pulse ✓

Both outputs described.

Condone – max counter value for 10th pulse.

Accept: both counters count from 0–9

OR both counters count to 10

2

(b) Duty cycle:

From oscilloscope $t_{on} = 3 \text{ div @ } 50 \mu\text{s / div} = 150 \mu\text{s}$

OR

$t_{off} = 2 \text{ div @ } 50 \mu\text{s / div} = 100 \mu\text{s} \checkmark$

$$\frac{t_{on}}{(t_{on} + t_{off})} \times 100 = 60\% \quad \text{OR} \quad 0.6 \quad \checkmark$$

(accept 'divisions' to signify the values of t_{on} and t_{off})

Frequency:

From CRO $t_p = 5 \text{ div @ } 50 \mu\text{s / div}$

$t_p = 250 \mu\text{s}$

$$f = 1/t_p = 4 \text{ kHz} \checkmark$$

Only 1 mark for:

either of t_{on} or t_{off} correct but duty cycle wrong

OR

correct use of both wrong t_{on} and t_{off}

One mark for:

correct use of their $t_{on} + t_{off}$

3

(c) **BCD:** $Q_2 = 600 / 10 = 60 \text{ Hz} \checkmark$

(only one pulse is produced in 10 clock pulses at Q_2)

Johnson: $Q_2 = 600 / 10 = 60 \text{ Hz} \checkmark$

2

[7]