


A LEVEL PHYSICS

WORKED SOLUTIONS


7.4. Capacitance MCQ



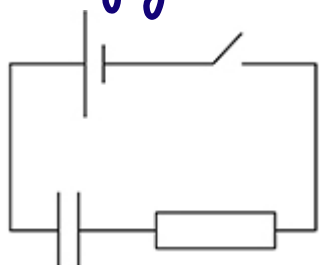1. The capacitor in the circuit is initially uncharged.
 The switch is closed at time $t = 0$ *∴ charging*



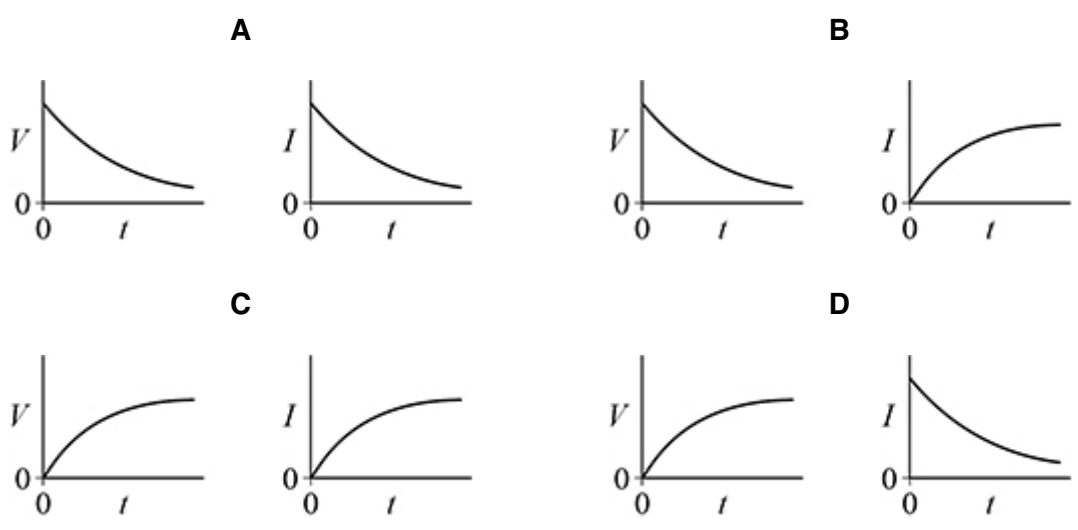Which pair of graphs shows how the potential difference V across the capacitor and the current I in the circuit change with time t ?



- A
- B
- C
- D

V increases
Q increases
I decreases

(Total 1 mark)

2. When a parallel-plate capacitor is connected across a battery, the energy stored in the capacitor is W .

The battery remains connected as the distance between the capacitor plates is halved.

What is the energy now stored in the capacitor?

A $0.5W$

B W

C $2W$

D $4W$

$$W = \frac{1}{2} QV = \frac{1}{2} Q \frac{E}{d} \quad W \propto \frac{1}{d}$$

$$d \rightarrow \frac{d}{2} \quad W \rightarrow 2W$$

(Total 1 mark)

3. An uncharged capacitor is connected to a power supply which supplies a constant current of $10 \mu\text{A}$.

After 100 ms, the potential difference across the capacitor is 5.0 kV.

What is the capacitance of the capacitor?

A $2.0 \times 10^{-10} \text{ F}$

B $4.0 \times 10^{-10} \text{ F}$

C $2.5 \times 10^9 \text{ F}$

D $5.0 \times 10^9 \text{ F}$

$$C = \frac{Q}{V} = \frac{It}{V} = \frac{10 \times 10^{-6} \times 100 \times 10^{-3}}{5.0 \times 10^3}$$

$$C = 2.0 \times 10^{-10}$$

(Total 1 mark)

4. A parallel-plate capacitor is made using a sheet of dielectric material between, and in contact with, two plates.

The properties of four sheets of dielectric material are shown.

$$C = A\epsilon_0\epsilon_r/d$$

Which sheet will produce the maximum capacitance?

$$C \propto \epsilon_r/d$$

Sheet	Relative permittivity	Thickness / mm
<u>A</u>	2	0.40
B	3	0.90
C	4	1.0
D	6	1.6



5



3.33



4



3.75

(Total 1 mark)

5. A parallel-plate capacitor is made by inserting a sheet of dielectric material between two plates. Both plates are in contact with the sheet.

Which relative permittivity and sheet thickness give the greatest capacitance?

	Relative permittivity	Thickness / mm
<u>A</u>	2	0.40
B	3	0.90
C	4	1.0
D	6	1.6



Same question as Q4 above

(Total 1 mark)

6. A $10 \mu\text{F}$ capacitor stores 4.5 mJ of energy. It then discharges through a 25Ω resistor.

What is the maximum current during the discharge of the capacitor?

A 1.2 A

B 18 A

C 30 A

D 36 A

$$W = \frac{1}{2} CV^2 \quad V = \sqrt{\frac{2W}{C}} = \sqrt{\frac{2 \times 4.5 \times 10^{-3}}{10 \times 10^{-6}}}$$

$$V = 30V$$

$$I = \frac{V}{R} = \frac{30}{25} = 1.2 \text{ A}$$

(Total 1 mark)

7. A $1.0 \mu\text{F}$ capacitor is charged for 20 s using a constant current of $10 \mu\text{A}$.

What is the charge collected by the sphere each second?

Question is confusing!

A $5.0 \times 10^{-3} \text{ J}$

energy?

B $1.0 \times 10^{-2} \text{ J}$

C $2.0 \times 10^{-2} \text{ J}$

D $4.0 \times 10^{-2} \text{ J}$

$$W = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(It)^2}{C}$$

$$W = \frac{1}{2} \frac{(10 \times 10^{-6} \times 20)^2}{1.0 \times 10^{-6}} = 2.0 \times 10^{-2} \text{ J}$$

(Total 1 mark)

8. A $1.0 \mu\text{F}$ capacitor initially stores $15 \mu\text{C}$ of charge. It then discharges through a 25Ω resistor.

What is the maximum current during the discharge of the capacitor?

A 0.60 mA

B 1.2 mA

C 0.60 A

D 1.2 A

$$V = \frac{Q}{C} = \frac{15 \times 10^{-6}}{1.0 \times 10^{-6}} = 15V$$

$$I = \frac{V}{R} = \frac{15}{25} = 0.60 \text{ A}$$

(Total 1 mark)

9. The initial potential difference across a capacitor is V_0 . The capacitor discharges through a circuit of time constant T . The base of natural logarithms is e .

What is the potential difference across the capacitor after time T ?

- A $\frac{V_0}{e}$ $V = V_0 e^{-\frac{t}{T}}$
- B** $\frac{V_0}{e}$ $t = T$
- C $V_0 e$ $V = V_0 e^{-1} = \frac{V_0}{e}$
- D $V_0 \ln 2$

(Total 1 mark)

10. An air-filled parallel-plate capacitor is charged from a source of emf. The electric field has a strength E between the plates. The capacitor is disconnected from the source of emf and the separation between the isolated plates is doubled.

What is the final electric field between the plates?

- A $2E$ *Not sure about this one!*
- B** E *I make it E/2 not E*
- C $\frac{E}{2}$
- D $\frac{E}{4}$

(Total 1 mark)

11. A parallel-plate capacitor has square plates of length l separated by distance d and is filled with a dielectric.

A second capacitor has square plates of length $2l$ separated by distance $2d$ and has air as its dielectric.

Both capacitors have the same capacitance.

What is the relative permittivity of the dielectric in the first capacitor?

$$C = A \epsilon_0 \epsilon_r / d$$

A $\frac{1}{2}$

$$\frac{\epsilon_{r1}}{\epsilon_{r2}} = \frac{d_1}{d_2} \cdot \frac{A_2}{A_1}$$

B 1


C 2

$$\frac{\epsilon_{r1}}{\epsilon_{r2}} = \frac{d}{2d} \cdot \frac{4l^2}{l^2} = \frac{1}{2} \times 4 = 2$$

D 8

(Total 1 mark)

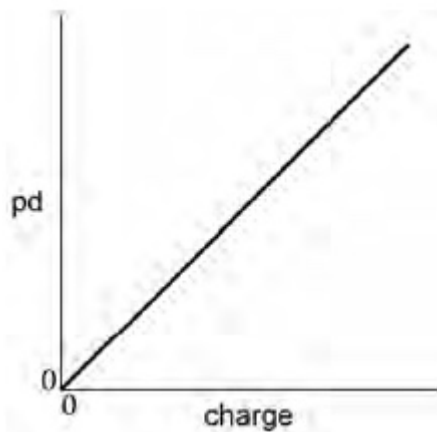12. The graph shows the variation of potential difference (pd) with charge for a capacitor while it is charging.



$$C = \frac{Q}{V} = \frac{1}{\text{gradient}}$$

gradient = constant

$\therefore C = \text{constant}$

Which statement can be deduced from the graph?

A The charging current is constant.

B The energy stored in the capacitor increases uniformly with time.

C The capacitance of the capacitor is constant.

D The power supply used to charge the capacitor had a constant terminal pd.

(Total 1 mark)

13.

A capacitor of capacitance $120 \mu\text{F}$ is charged and then discharged through a $20 \text{ k}\Omega$ resistor.

What fraction of the original charge remains on the capacitor 4.8 s after the discharge begins?

A 0.14



$$\frac{Q}{Q_0} = e^{-t/RC}$$

B 0.37



$$= e^{-4.8 / (20 \times 10^3 \times 120 \times 10^{-6})}$$

C 0.63



$$= e$$

D 0.86



$$= 0.135$$

$$= 0.14$$

(Total 1 mark)

14.

A capacitor consists of two parallel square plates of side l separated by distance d .

The capacitance of the arrangement is C .

What is the capacitance of a capacitor with square plates of side $2l$ separated by a distance $\frac{d}{2}$?

A C



$$C = A \epsilon_0 \epsilon_r / d$$

B $2C$



C $4C$



$$\frac{C_2}{C_1} = \frac{A_2}{A_1} \cdot \frac{d_1}{d_2} = \frac{4l^2}{l^2} \cdot \frac{d}{d/2} = 4 \times 2 = 8$$

D $8C$



(Total 1 mark)

15.

A capacitor of capacitance C has a charge of Q stored on the plates. The potential difference between the plates is doubled.

What is the change in the energy stored by the capacitor?

A $\frac{Q^2}{2C}$



$$E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

B $\frac{Q^2}{C}$



$$\Delta E = E_2 - E_1$$

C $\frac{3Q^2}{2C}$



$$= \frac{1}{2} C (2V)^2 - \frac{1}{2} CV^2$$

D $\frac{2Q^2}{C}$



$$= 2CV^2 - \frac{1}{2} CV^2 = \frac{3}{2} CV^2$$

(Total 1 mark)

$$\frac{3}{2} CV^2 = \frac{3}{2} \frac{Q^2}{C}$$