

M1.(a) $V_{-} \left(= 12 \times \frac{6}{9} \right) = 8 \text{ V (1)}$

1

(b) at 0 °C, $R_{th} = 100 \text{ } (\Omega) \text{ (1)}$
 $R_1 = (2 \times R_{th}) = 200 \text{ } \Omega \text{ (1)}$

2

(c) (i) $R_2 = \left(\frac{12 - 2}{20 \times 10^{-3}} \right) \text{ (1)}$
 $= 500 \text{ } \Omega \text{ (1)}$

(ii) (use of $P = I^2 R$ gives) $P = (20 \times 10^{-3})^2 \times 500 \text{ (1)}$
 $= 0.20 \text{ W (1)}$
 (allow C.E. for value of R_2 from (i))

4

(d) $510 \text{ } \Omega$
 (allow C.E. for value of R_2 from (c)(i))

1

[8]

M2.(a) $V_{-} = 12 \times \frac{30}{46} \text{ (1)}$
 $= 7.8 \text{ V (1)}$

2

(b) (i) between V_{out} and 0 V (1)
 (or from +12 V to V_{out})
 correct direction and resistor (1)

(ii) (since $V_{in} - V_{out} = -12 \text{ V}$ (12 V across LED) (1)
 (or alternative)

- (iii) voltage across $R = (12 - 2) = 10$ (V) **(1)**
 $10 = 25 \times 10^{-3} \times R$ gives $R = 400 \Omega$ **(1)**
 (or alternatively $22 = 25 \times 10^{-3}$ to give $R = 880 \Omega$)

5

- (c) to switch LED voltage at B = 7.8 (V) **(1)**

$$R_{\text{LDR}} \text{ given by } 7.8 = \frac{12 \times 47}{47 + R} \text{ or}$$

$$R_{\text{LDR}} = 25.3 \text{ k}\Omega$$

light level = 30 lux **(1)**

max 3

[10]

- M3.(a)** high input impedance
 very large voltage gain
 low output impedance
- any two **(1) (1)**

2

- (b) (i) circuit diagram to show: correct feedback and output **(1)**
 correct inputs **(1)**

- (ii) $R_a \geq 1 \text{ k}\Omega$ **(1)**
 gives $R_f = 150 \text{ k}\Omega$ **(1)**

4

- (c) (i) fraction of output fed back through R_f **(1)**
 is 180° out of phase with input **(1)**
- (ii) increased stability or less distortion or controlled gain **(1)**
- (iii) range of frequencies within which voltage gain
 does not fall by $1/\sqrt{2}$ or power by $1/2$ **(1)**

- (iv) bandwidth given by gain of $\frac{22}{\sqrt{2}} = 16$ **(1)** (15.6)

horizontal line at gain = 16 and inside curve

max 5

[11]

