

- M1.(a)** (i) D to inv. output, ✓
 CK to inv. output, ✓
 Resets together ✓
 label astable input ✓
 three labelled outputs ✓

5

- (ii) AND gate, ✓
 output to Reset, ✓
 inputs from Y and Z ✓

3

(b)

Binary counter output		Dice output	
Denary	Binary Z Y X	Dice number	Lamps on
0	0 0 0	1	D
1	0 0 1	2	A
2	0 1 0	3	D, A
3	0 1 1	4	A, C
4	1 0 0	5	A, C, D
5	1 0 1	6	A, B, C

one per correct answer ✓ ✓ ✓ ✓ ✓

5

[13]