

**M1.(a)** It is not actually connected to 0V ✓

OR

Operational amplifier has a very large open loop gain

The voltage between  $V_+$  and  $V_-$  inputs has to be zero [or tiny ] otherwise will saturate ✓

2

(b)  $V_{OUT} = -270K / 22K \times V_{IN} = -12.3 V_{IN}$

OR

$$V_{IN} = 50 \times 0.01 = 0.5 \text{ V } \checkmark$$

$$V_{OUT} = -12.3 \times 0.5 = -6.1 \text{ V } \checkmark$$

2

(c) At 122 °C  $V_{OUT} = 122 \times 0.01 \times 12.3 = 15.0 \text{ V } \checkmark$

so any higher temp will give no further increase in  $V_{OUT}$  ✓ WTTE

OR

$$\text{Max } V_{IN} = 15.0 / 12.3 = 1.22 \text{ V } \checkmark$$

$$\text{Max input temperature} = 1.22 / 0.01 = 122 \text{ }^\circ\text{C } \checkmark$$

2

(d) Level is fixed by controlling the pd at the + input)

OR

Turns off at higher temperature if V at + terminal higher ✓

Output of the circuit is determined by  $R_f / R_i (V_2 - V_1)$  ✓

When  $V_1 = V_2$  the output changes from + to - (causing heater to switch off) ✓

3

[9]

**M2.(a)** (i) negative feedback: part or all of the output is fed back to the input

180° out of phase (1)

achieved through  $R_f$  (1)


(ii) greater stability  
less distortion

any two (1) (1)

increased bandwidth  
gain predictable

4

(b)

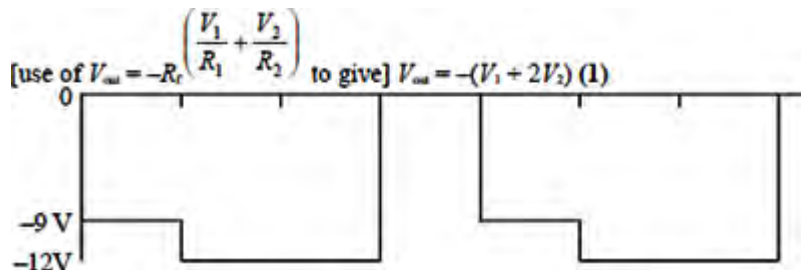

negative values (1)  
correct 9 V and 12 V (1)  
saturation (1)  
repeated (1)

max 4

[8]

**M3.(a)**  $I_a = \frac{1.2}{6(k\Omega)} = 0.2 \text{ mA}$  (1)

$I_b = 0.3 \text{ mA}$  and  $I_c = 0.6 \text{ mA}$  (1)  
correct direction of current shown (1)

(b) current through  $R_f = 1.1 \text{ (mA)}$  gives  $V_{out} = 1.1 \times 10^{-3} \times 10 \times 10^3 = 11 \text{ V}$  (1)  
negative value (1)

(c)  $V_{out} (22 \text{ V}) >$  supply voltage [or saturated] (1)  
 $V_{out} = (-)15 \text{ V}$  (1)

[6]